
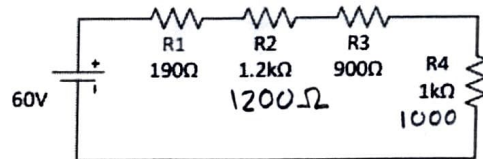


Intro to Digital Fabrication

Electronics Problem Set 1

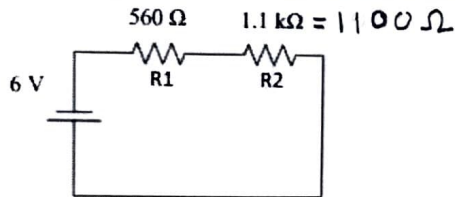1 Use the following circuits to practice analyzing series resistance. Determine the requested information and sketch the minimized equivalent circuit



$$I = \frac{V}{R}$$

$$V = IR$$

$$P = IV$$

$$R_T = 1660 \Omega$$

$$I_T = 3.614 \text{ mA}$$

$$V_{R1} = 2.024 \text{ V}$$

$$V_{R2} = 3.976 \text{ V}$$

$$P_{R1} = 7.316 \text{ mW}$$

$$P_{R2} = 14.371 \text{ mW}$$

$$P_T = 21.687 \text{ mW}$$

Sketch the equivalent circuit:



$$R_T = 3290 \Omega$$

$$I_T = .01824 \text{ A}$$

$$V_{R1} = 3.465 \text{ V}$$


$$V_{R2} = 21.884 \text{ V}$$

$$V_{R3} = 16.413 \text{ V}$$

$$V_{R4} = 18.237 \text{ V}$$

$$P_T = 1.0942 \text{ W}$$

Sketch the equivalent circuit:

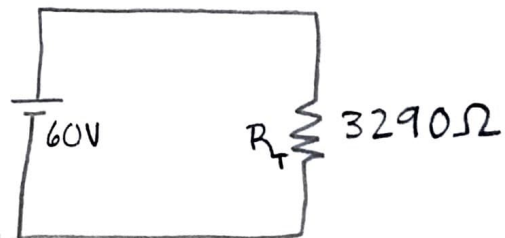

2

Use the following circuits to practice analyzing parallel resistance. Determine the requested information and sketch the minimized circuits.

$$I = \frac{V}{R}$$

$$P = I V$$

$$R_T = 9.706 \Omega$$

$$I_T = .515 A$$


$$I_{R1} = .5 A$$

$$I_{R2} = 15.151 mA$$

$$P_{R1} = 2.5 W$$

$$P_{R2} = .0757 W$$

$$P_T = 2.576 W$$

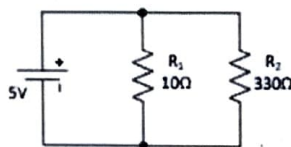

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



$$R_T = 58.441 \Omega$$


$$I_T = .616 A$$

$$I_{R1} = .4 A$$

$$I_{R2} = .18 A$$

$$I_{R3} = .036 A$$

$$P_T = 22.176 W$$

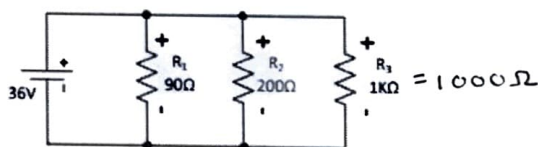

$$R_T = \frac{1}{\frac{1}{90} + \frac{1}{200} + \frac{1}{1000}}$$



Is the total resistance larger than the largest single resistor or smaller than the smallest resistor? Is this what you would have expected?

The total resistance is smaller than the smallest resistor which makes sense because the charge gets distributed among the different paths.

Does the total current equal the sum of the currents through each resistor?

$$I_{R1} + I_{R2} = I_T$$

$$.5 + .015 = .515 A$$

$$I_{R1} + I_{R2} + I_{R3} = I_T$$

$$.4 + .18 + .036 = .616 A$$

yes the sum of the currents through each resistor equals the total.

$$R_{3+4} = \frac{1}{\frac{1}{20} + \frac{1}{50}} = 14.286$$

$$R_T = R_1 + R_2 + R_{3+4}$$

3 Analyze the circuits to determine the following. Sketch the minimized equivalent circuit.



$$I = \frac{V}{R}$$

$$P = IV$$

$$R_T = 94.286 \Omega$$

$$I_T = .106 A$$

$$P_T = 1.061 W$$

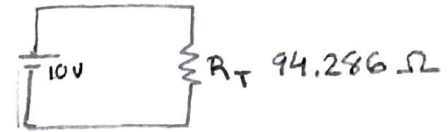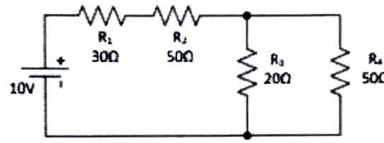


$$R_{2+3} = \frac{1}{\frac{1}{3300} + \frac{1}{90}}$$

$$R_T = 134.611 \Omega$$



$$I_T = 89.146 mA$$

$$P_T = 1.07 W$$

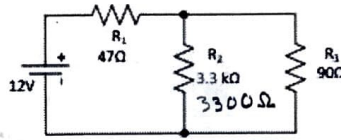

$$R_T = R_1 + R_{2+3}$$

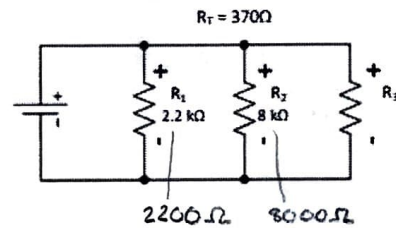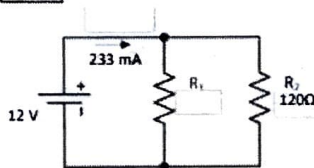4 Determine the value for the missing component in the following circuits.



$$R_1 = 90.226 \Omega$$

$$R_3 = 470.996 \Omega$$

$$I_T = .233 A$$

$$\frac{V_2}{R_2} = I_2 = \frac{12}{120} = .1 A$$

$$I_T - I_2 = I_1$$

$$.233 - .1 = .133$$

$$R_1 = \frac{V}{I_1} = \frac{12}{.133}$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$\frac{370}{1} = \frac{1}{\frac{1}{2200} + \frac{1}{8000} + \frac{1}{R_3}}$$

$$.0005795$$

$$370 \left(.0005795 + \frac{1}{R_3} \right) = 1$$



$$\frac{1}{R_3} = \frac{1}{370} - .0005795$$

$$\frac{1}{R_3} = .00212$$

$$R_{1+2} = \frac{1}{\frac{1}{2} + \frac{1}{2}} = 1$$

$$R_T = R_{1+2} + R_3 = 1 + 3$$

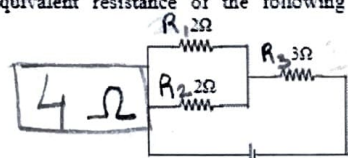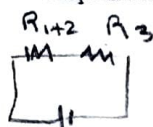
5 Calculate the equivalent resistance of the following compound circuit



6 Calculate the equivalent resistance R and the total current I.

$$2\Omega = R_T$$

$$2A = I_T$$

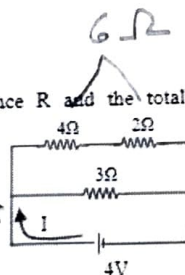

$$R_T = \frac{1}{\frac{1}{3} + \frac{1}{(4+2)}} = 2$$

$$V_1 = I_T R_1 = 4 \cdot 3 = 12$$

$$V_1 = V_T = V_2 + 3$$

$$I_T = \frac{V_T}{R_T} = \frac{12}{2} = 6$$

$$I_{2+3} = I_T - I_1$$

$$2 = 6 - 4$$


$$V_2 = I_{2+3} R_2$$

$$4 = 2 \cdot 2$$

7 Calculate the equivalent resistance R and the total current I

$$\frac{1}{\frac{1}{4} + \frac{1}{2}} + 1 = R_T$$

$$I_T = \frac{V}{R} = \frac{7}{2.33}$$

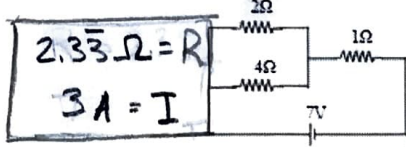


8 Calculate the total current I, total voltage V and V2

$$I_T = 6A$$

$$V_T = 12V$$

$$V_2 = 4V$$

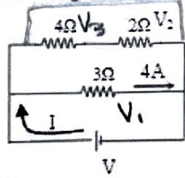


10 Calculate the R2 and I2

$$I_2 = I_T - I_1$$

$$A_2 = V_2 / I_2$$


$$I_2 = .067A$$

$$R_2 = 30\Omega$$

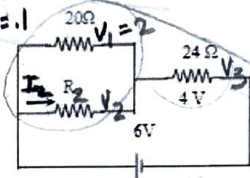

9 Calculate the equivalent resistance R and the total current I
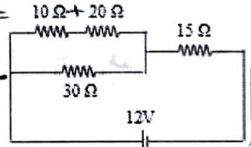
$$R_T = \frac{1}{\frac{1}{30} + \frac{1}{30}} + 15 = 30\Omega$$



$$I = \frac{V}{R} = \frac{12}{30} = .4A$$


$$R = 30\Omega$$

$$I = .4A$$

11 Calculate the I2, R3, the total current I

$$I_2 = \frac{V_2}{R_2} = \frac{3}{3}$$

$$I_T = I_1 + I_2$$

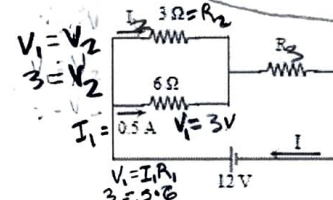

$$I_T = I_3 = \frac{4}{24} = .167A$$

$$V_T = V_{1+2} + V_3$$

$$6 = V_{1+2} + 4$$


$$I_3 = I_T$$

$$R_3 = V_3 / I_3 = \frac{9}{.15}$$

12 Calculate the total current I and total voltage V

$$I_T = I_1 + I_2$$

$$.1 + .1$$

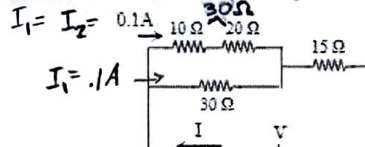

$$R_T = \frac{1}{\frac{1}{30} + \frac{1}{30}} + 15 = 30\Omega$$

$$V_T = I_T R_T$$

$$.2 \cdot 30$$

$$I_T = .2A$$


$$V_T = 6V$$

13 Calculate the total current I and total voltage V

$$R = \frac{1}{\frac{1}{60} + \frac{1}{20}} = 15\Omega$$

$$I_T = .4A$$

$$V_T = 12V$$

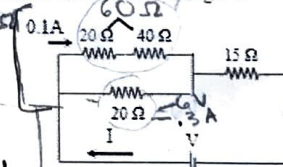

$$I R$$

$$V = .1 \cdot 60 = 6V$$

$$R_T = 15 + 15 = 30\Omega$$

$$V_T = I_T R_T$$

$$.4 \cdot 30$$

14 If R1 = R2, calculate the R1, I2, and the total current I

$$I_1 = I_2$$

$$I_T = I_3 = I_1 + I_2$$

$$.1 = 2I_1$$


$$.05 = I_1 = I_2$$

$$R_T = \frac{V_T}{I_T} = \frac{10}{.1} = 100\Omega$$

$$R_T = 40 + \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$100 - 40 = \frac{1}{\frac{2}{R_1}}$$

$$60 = \frac{R_1}{2} \quad R_1 = 120$$

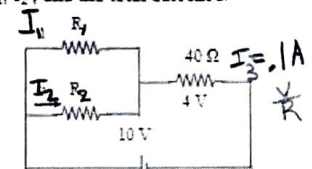

$$R_1 = 120\Omega$$

$$I_2 = .05A$$

$$I_T = .1A$$

15 Use the diagram to calculate a) the total resistance in the circuit, b) the total current through the circuit, c) the total power the circuit consume, and d) the current through R2 (where R1 = 10Ω, R2 = 30Ω, R3 = 30Ω, R4 = 15Ω, V = 12V)

$$P = IV$$

$$.5 \cdot 12$$

$$R_2 = R_3$$

$$I_2 = I_3$$

$$I_T = I_2 + I_3$$


$$.3 = 2I_2$$

$$R_T = 40\Omega$$


$$I_T = .3A$$

$$P_T = 3.6W$$

$$I_2 = .15A$$

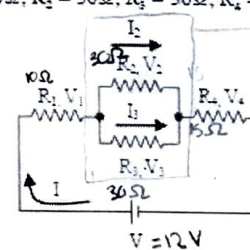

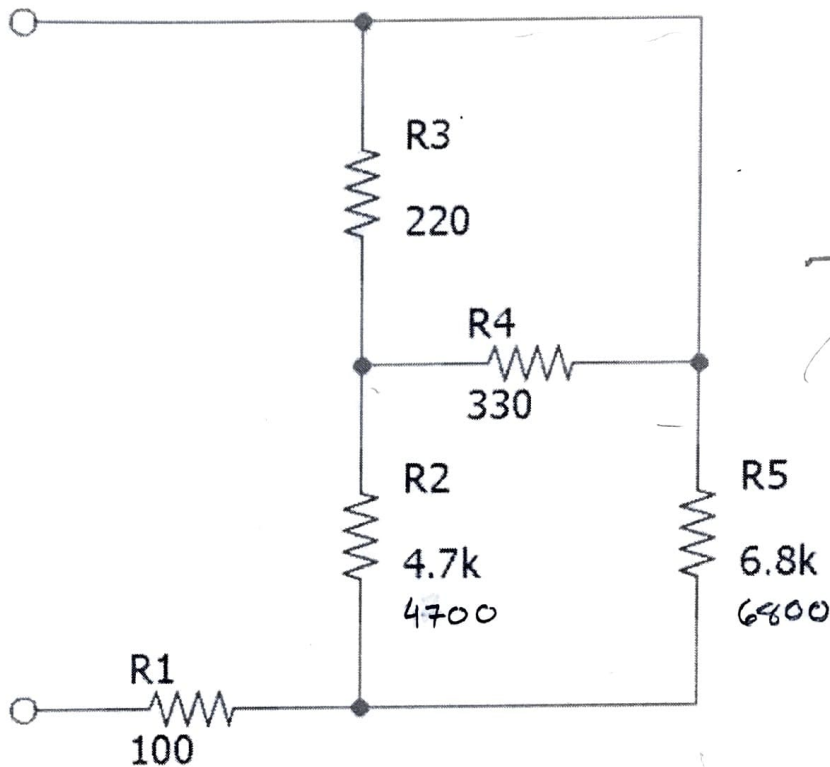Find the equivalent resistance for the following set of connected resistors:



$$R_{3+4} = \frac{1}{\frac{1}{220} + \frac{1}{330}} \approx 132 \Omega$$

$$R_{3+4+2} = 132 + 4700 = 4832 \Omega$$

$$R_{3+4+2+5} = \frac{1}{\frac{1}{4832} + \frac{1}{6800}} \approx 2824.759 \Omega$$

$$R_T = R_{3+4+2+5} + R_1$$

$$R_T = 2824.75 + 100$$

$$R_T = 2924.759 \Omega$$

